

Physics 204

Problems for Assignment 13

Due Friday, 25 April 2008

1 Cylindrical Capacitor

Consider two hollow concentric cylinders of length l with equal and opposite charge on them. The inner cylinder has a radius a and charge $+Q$ on it. The outer cylinder has a radius b and a charge $-Q$ on it. (Hint: See section 28-3 of your text.)

- (a) Use Gauss' law to compute the electric field for $r < a$, $a < r < b$, and $r > b$. Neglect edge effects.
- (b) Compute the the potential difference between the two cylinders.
- (c) Compute the capacitance of this cylindrical capacitor.

2 Spherical Capacitor

Consider two hollow concentric spheres with equal and opposite charge on them. The inner sphere has a radius a and charge $-Q$ on it. The outer sphere has a radius b and a charge $+Q$ on it. (Hint: See section 28-3 of your text.)

- (a) Use Gauss' law to compute the electric field for $r < a$, $a < r < b$, and $r > b$.
- (b) Compute the the potential difference between the two spheres.
- (c) Compute the capacitance of this spherical capacitor.

3 Multiple Capacitors

- (a) Show that the equivalent capacitance of multiple capacitors in series C_{eq} is given by $1/C_{eq} = \sum_i 1/C_i$
- (b) Show that the equivalent capacitance of multiple capacitors in parallel C_{eq} is given by $C_{eq} = \sum_i C_i$

(Hint: See section 28.4 of your text.)

4 Discharging a Capacitor

Consider a circuit with a charged capacitor, a resistor, and a switch (initially open) connected in series. (Hint: See section 28-9 of your text.)

- (a) What is the [differential] equation that describes the charge in this circuit after the switch is closed. Explain your signs carefully in this equation. (Hint: Use the loop rule.)
- (b) Guess a solution to this differential equation and verify that it is a solution by plugging it back in.
- (c) Complete Touchstone Example 28-5 from your text.

5 Touchstone Example 32-2: Two Inductors and Three Resistors

Figure 32-9a shows a circuit that contains three identical resistors with resistance $R = 9.0\ \Omega$, two identical ideal inductors with inductance $L = 2.0\ \text{mH}$, and an ideal battery with emf $\varepsilon = 18\ \text{V}$.

- (a) What is the current i through the battery just after the switch is closed?
- (b) What is the current i through the battery long after the switch has been closed?

6 Cummings 32.7: Inductors in Series

Two inductors L_1 and L_2 are connected in series and separated by a large distance.

- (a) Show that the equivalent inductance L_{eq} is given by $L_{eq} = L_1 + L_2$
- (b) Why must their separation be large for this relationship to hold?
- (c) What is the generalization for (a) for N inductors in parallel?

7 Cummings 32.10: Inductors in Parallel

Two inductors L_1 and L_2 are connected in parallel and separated by a large distance.

- (a) Show that the equivalent inductance L_{eq} is given by $1/L_{eq} = 1/L_1 + 1/L_2$
- (b) Why must their separation be large for this relationship to hold?
- (c) What is the generalization for (a) for N inductors in series?

8 Cummings 33.18: SHM

A 0.50 kg body oscillates in simple harmonic motion on a spring that, when extended 2.0 mm from its equilibrium has an 8.0 N restoring Force.

- (a) What is the angular frequency of oscillation?
- (b) What is the period of oscillation?
- (c) What is the capacitance of an LC circuit with the same period if L is chosen to be 5.0 H?